
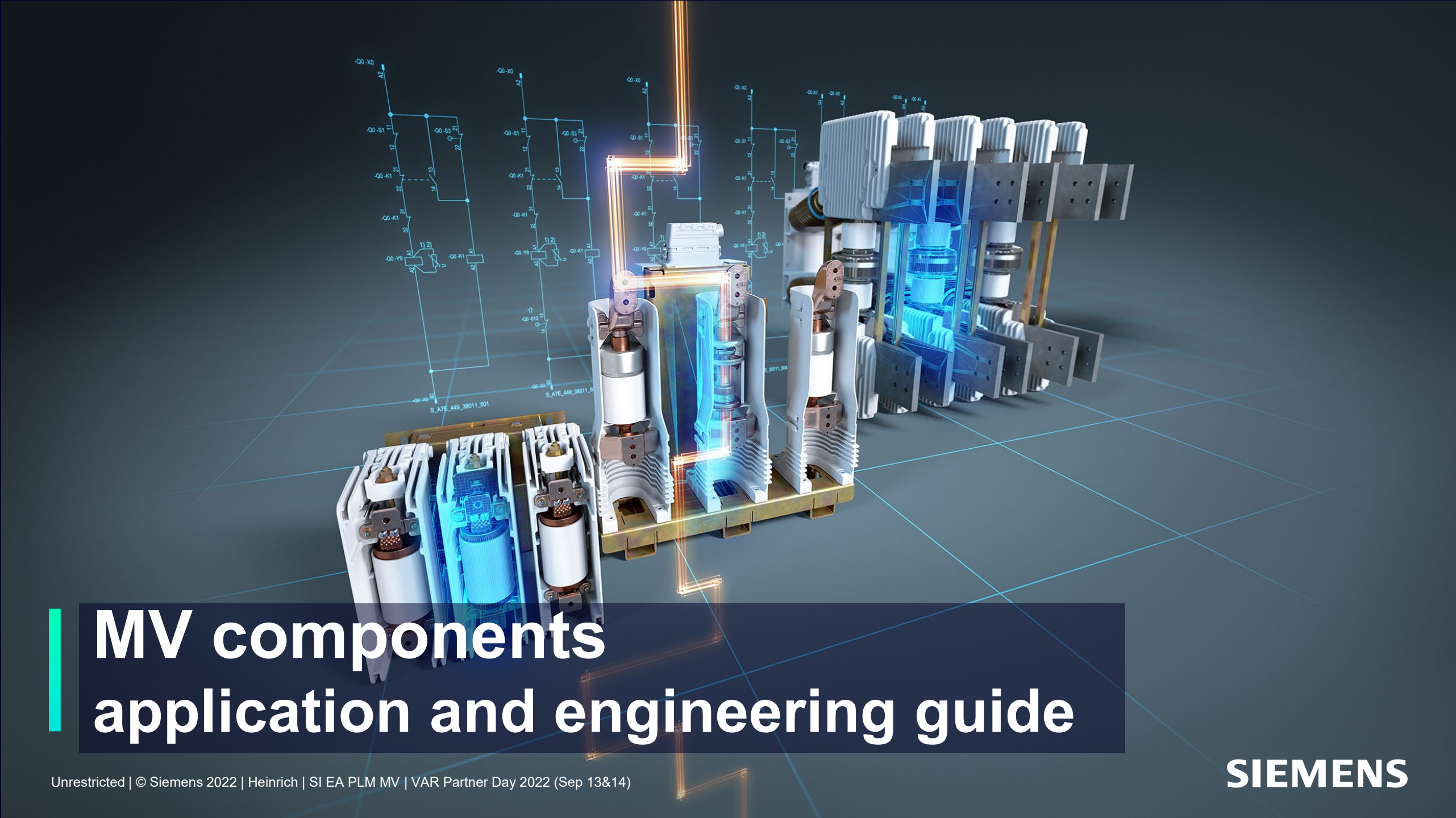


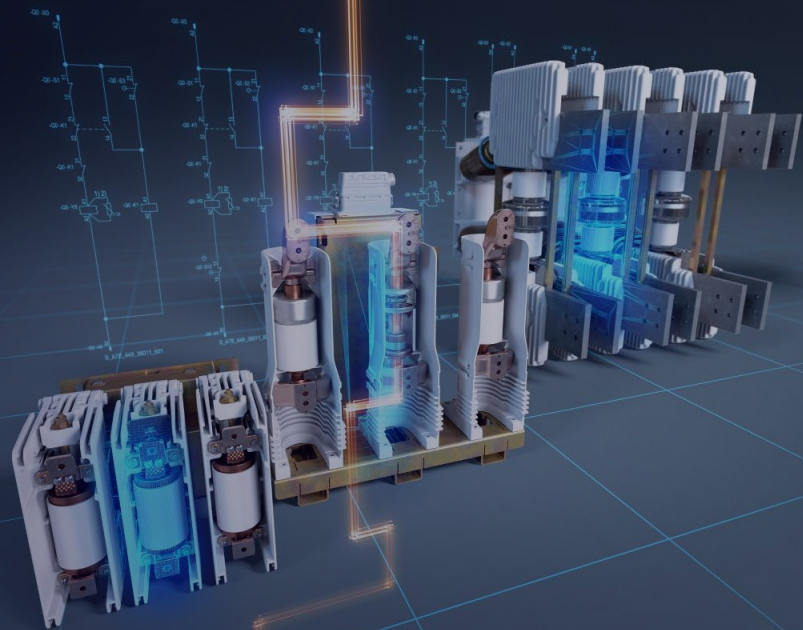

MV components application and engineering guide


MEDIUM VOLTAGE COMPONENTS – PRODUCT PORTFOLIO INDOOR



Vacuum circuit-breakers
for general applications



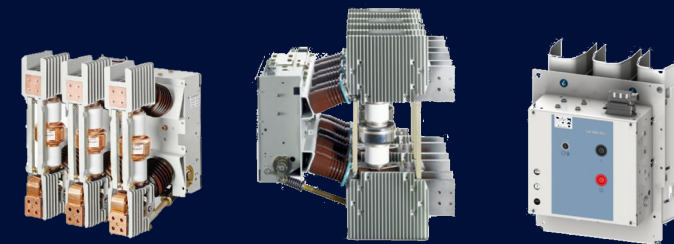Vacuum circuit-breakers
for special applications




Vacuum contactors



Vacuum interrupters




Auxiliary switches and
accessories

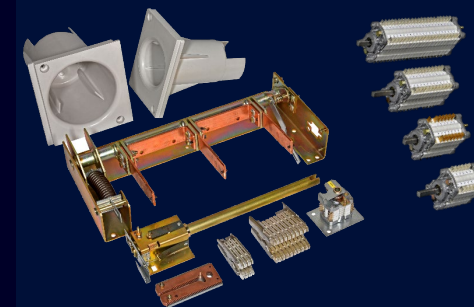

Rated Values


Influencing parameters on devices and switchgear

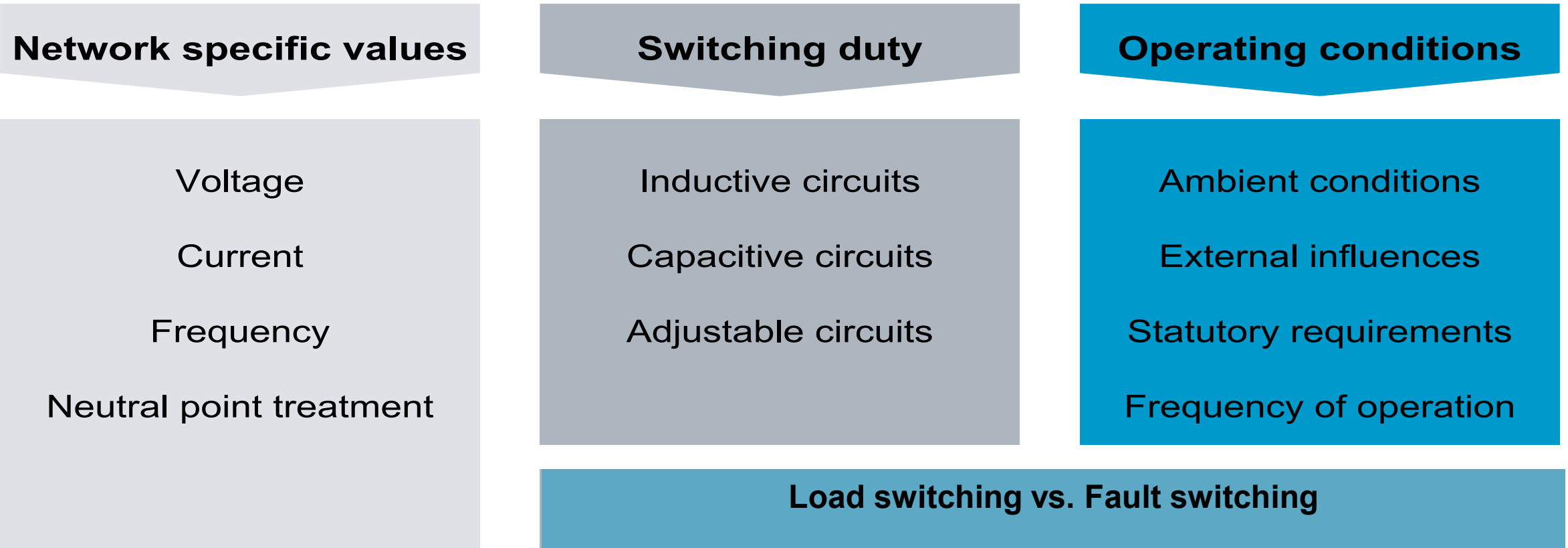A number of parameters have to be considered for selecting the right product



Medium-voltage switches are current-zero interrupters

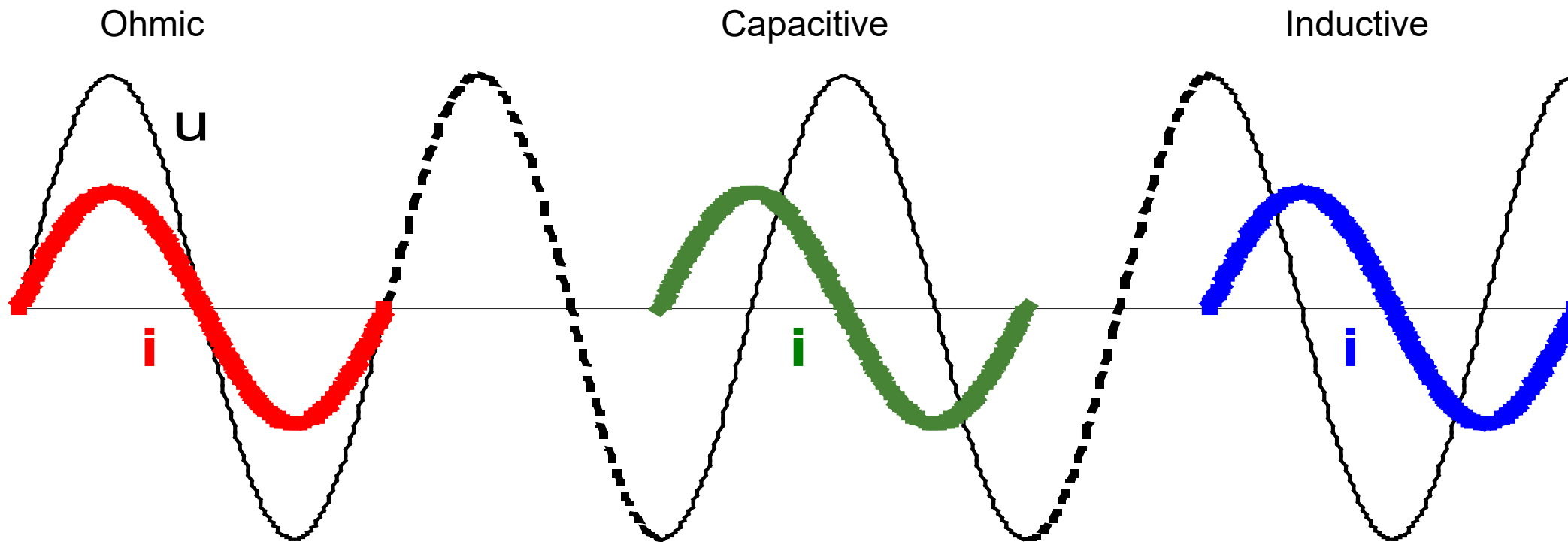Stationary phase angle between current and voltage



Inductive circuits



- In inductive circuits the current lags behind the voltage, $\cos \varphi < 0.3$.
- When interrupting inductive currents the electromagnetic energy remains stored in the inductance.
- The stored energy discharges by means of high-frequency oscillations in the circuit which has been switched-off.
- When switching off the following effects can be observed:
 - **(DC offset) at s.c. current interruption**
 - **Current chopping**
 - **Multiple re-ignitions**





Source: Maschinenfabrik Reinhausen

L1. Large inductive currents

Current and voltage in a short-circuit

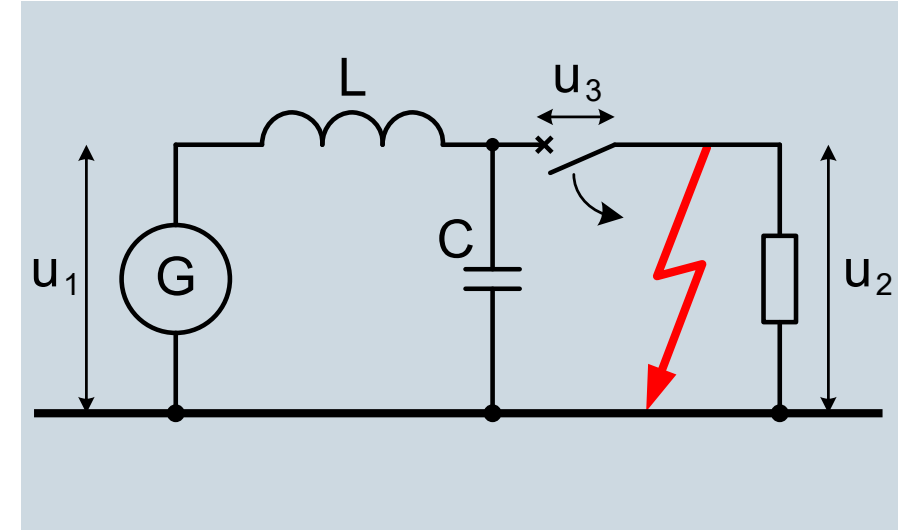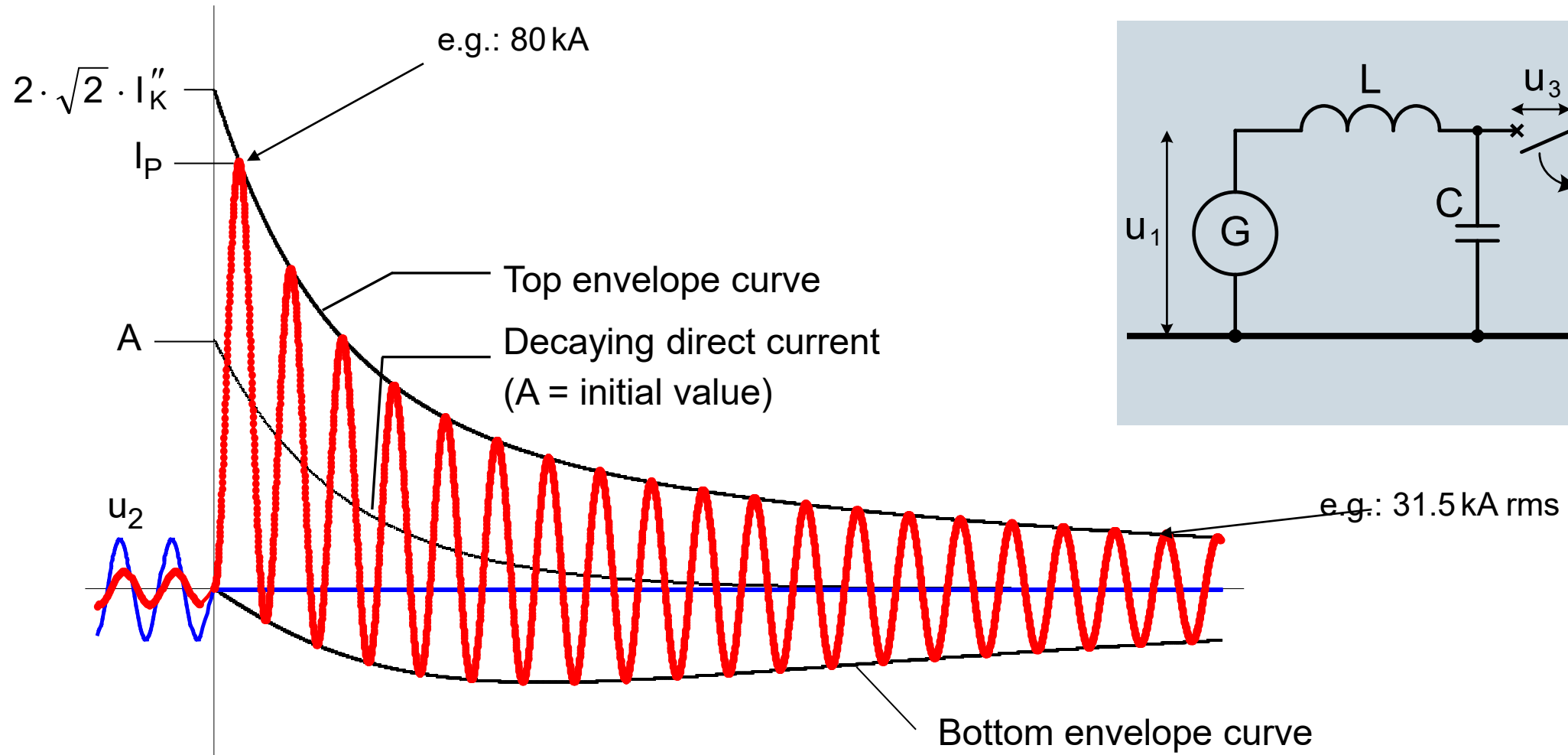

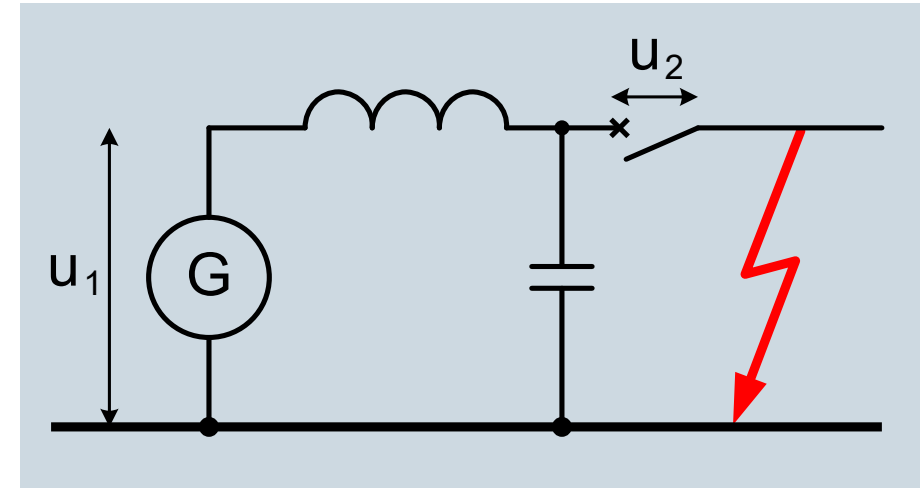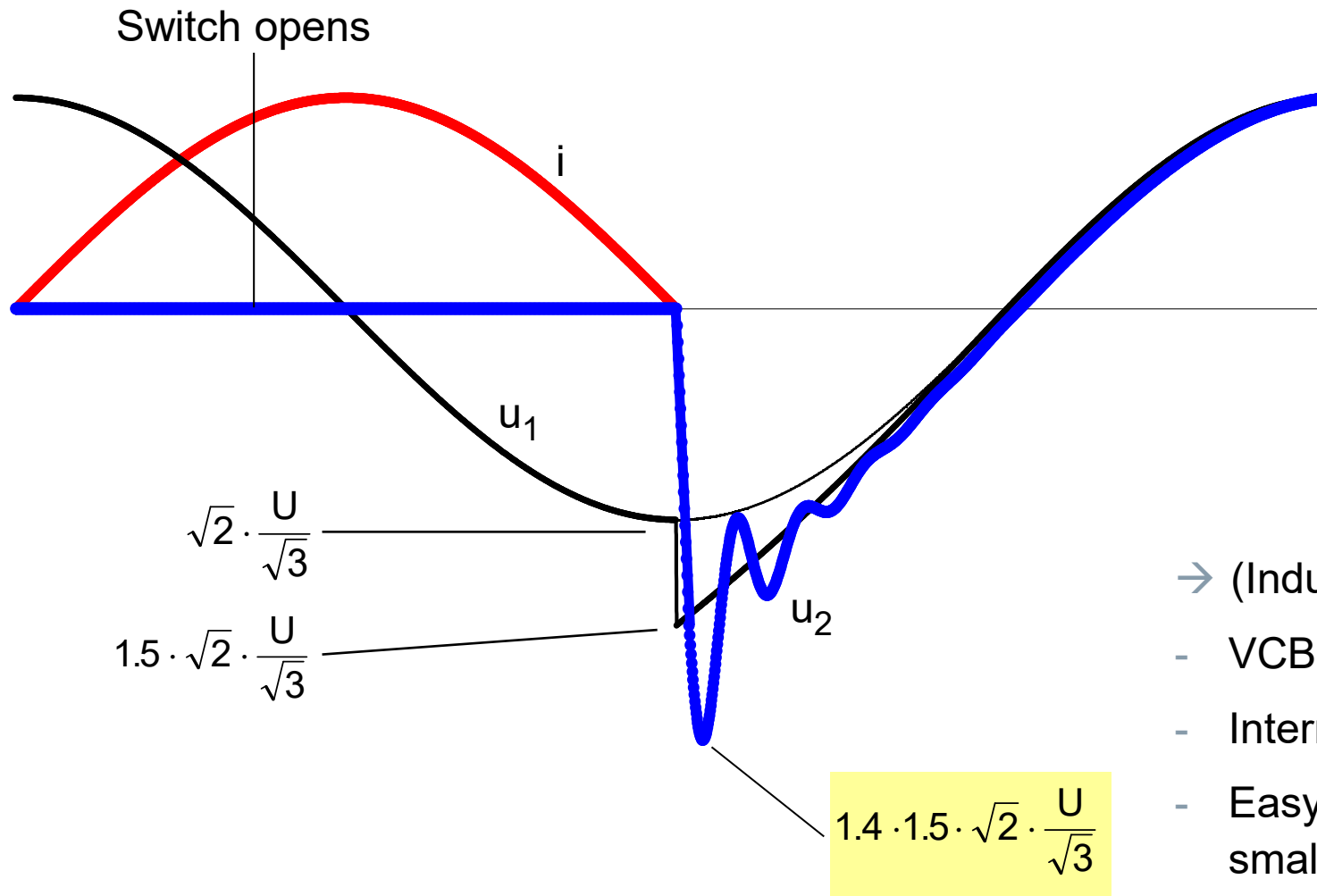
Transient recovery voltage (TRV) in the first pole to open / first pole to clear




- (Inductive) s.c. currents are the major duty of CB
- VCB are designed for it
 - Interrupt safely
 - Easy to cope with other requirements in test e.g. small critical currents, RRRV, reclosing, etc.

L2. Small inductive currents - chopping when breaking

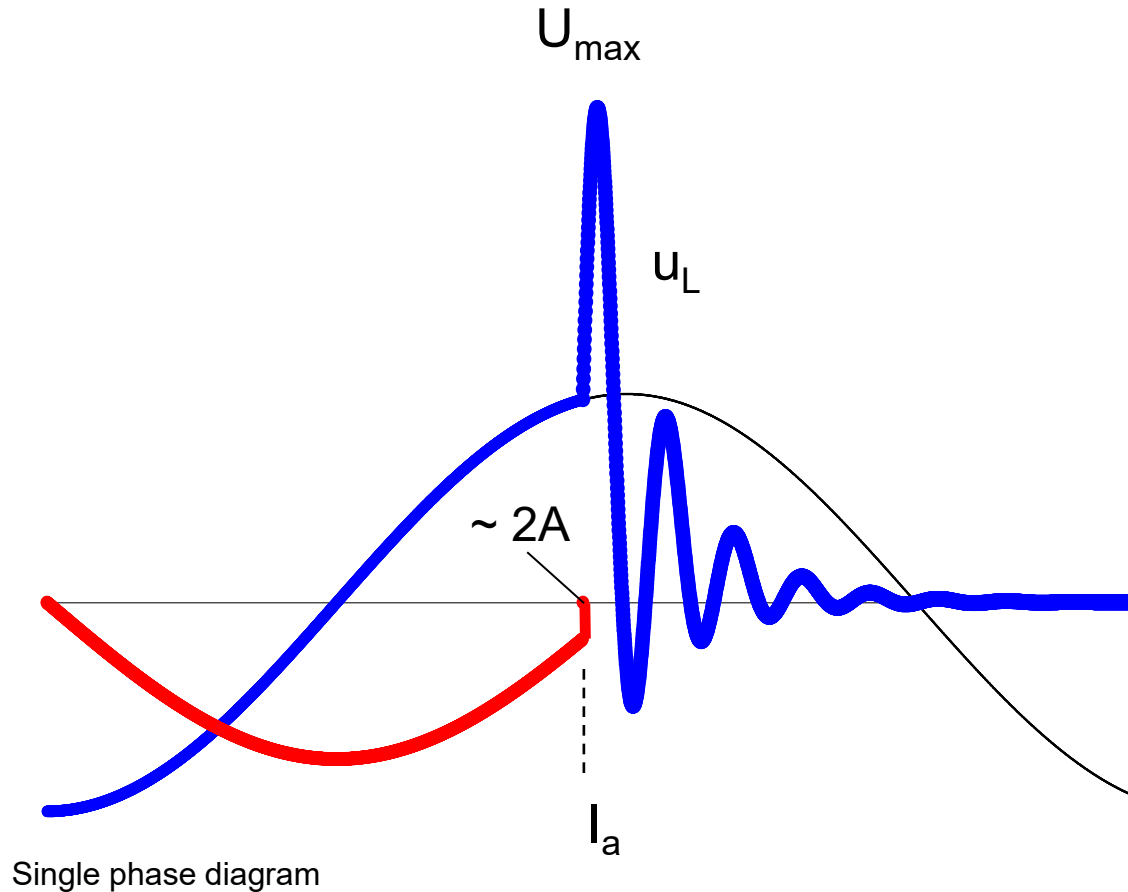
e. g. switching off unloaded transformers



Single line diagram

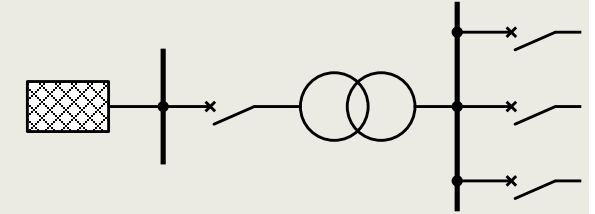

Equivalent circuit-diagram

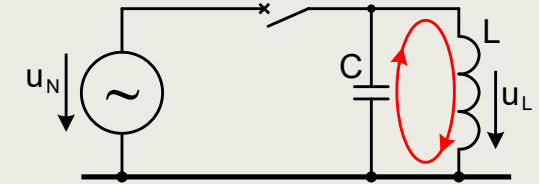

Formula for stored energy

$$\frac{1}{2} \cdot C \cdot u^2 = \frac{1}{2} \cdot L \cdot i^2$$

Maximum voltage at load


$$u_{\max} \approx \sqrt{\frac{L}{C}} \cdot i_a$$

L2. Small inductive currents

Replication of real installation conditions


Representative applications of transformers in industry and distribution networks

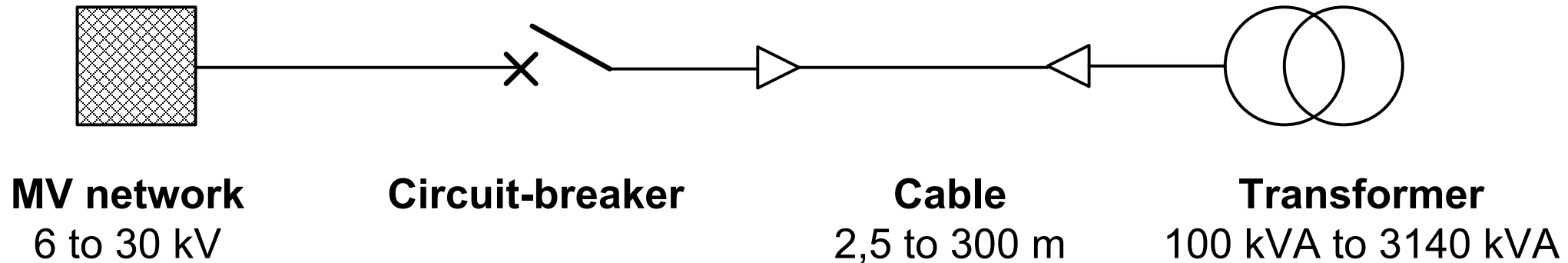- Typical distribution transformers (U_r , S_{rT} , u_k , vector group, oil and cast-resin insulation)
- Vacuum circuit-breakers
- Network voltage from 6 kV to 30 kV
- Cable lengths from 2.5 to 300 m




L2. Small inductive currents

Maximum overvoltage factors recorded

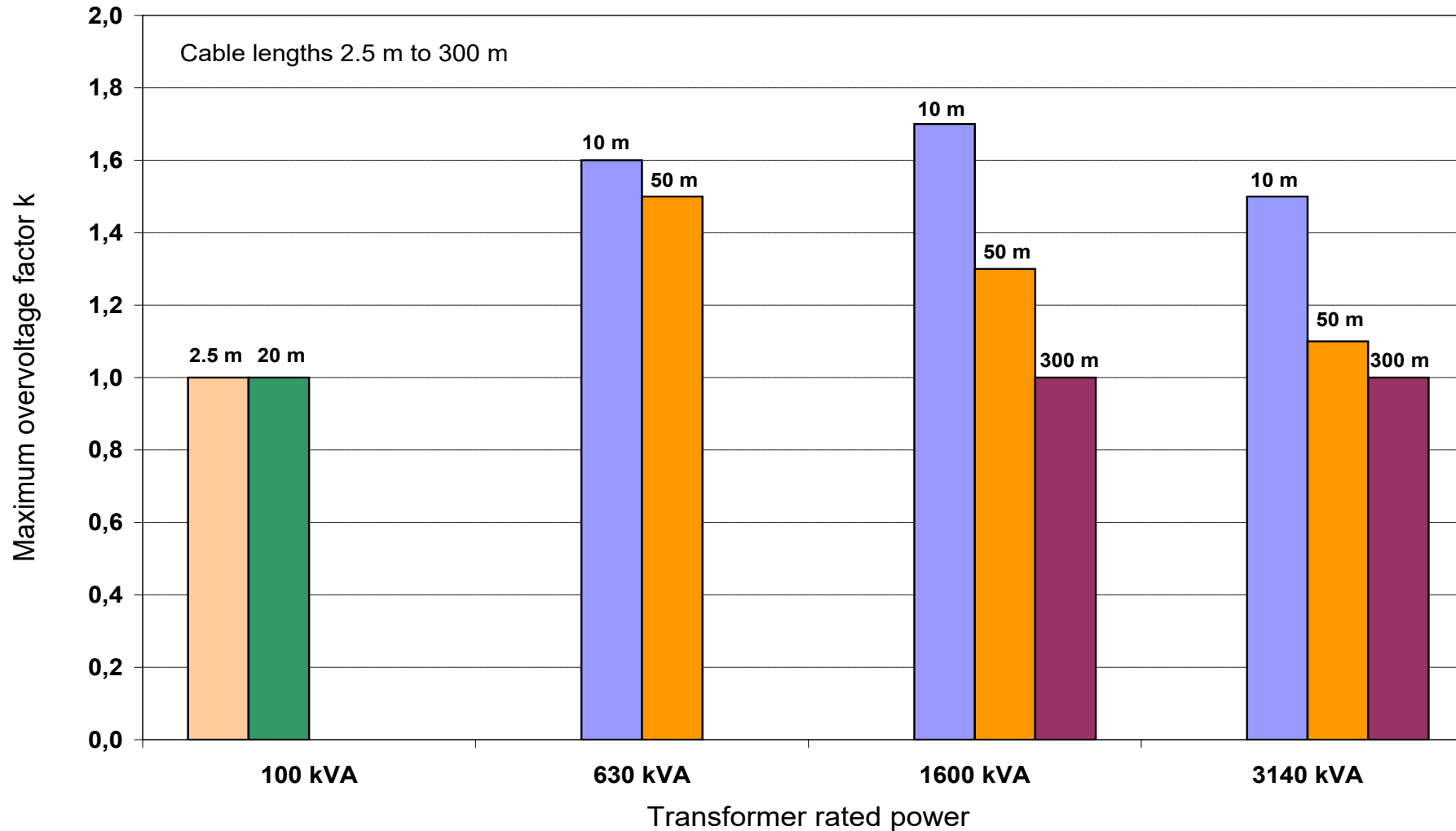


L3. Multiple re-ignitions – Principle

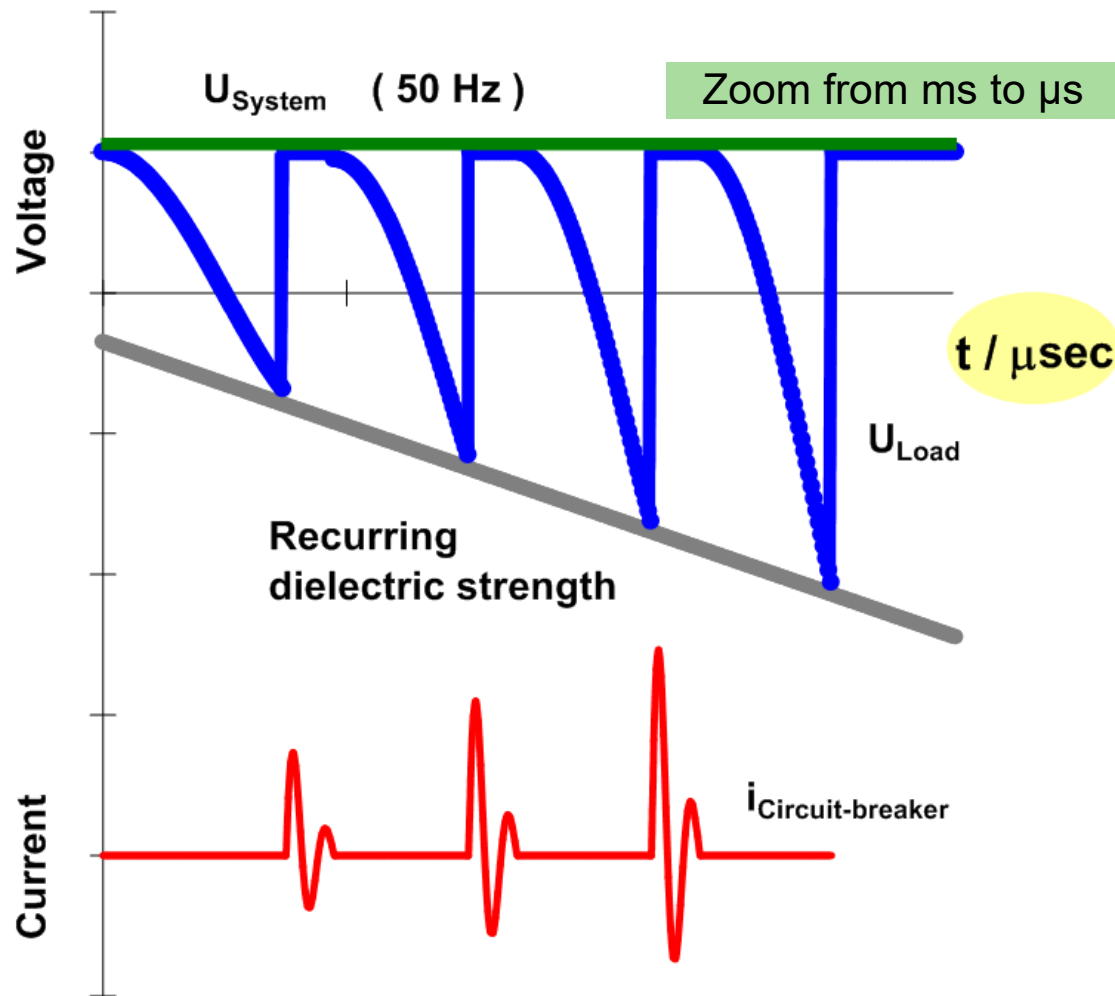


Preconditions for multiple re-ignitions:

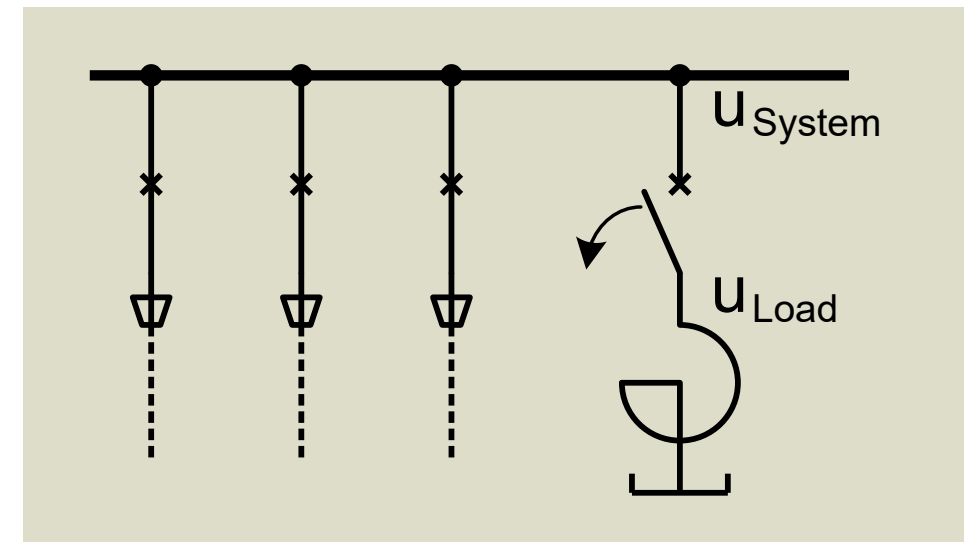- Breaking an inductive current
- Contact separation $< 0.5 \text{ ms}$ prior to current zero




Induced (virtual) current chopping due to multiple reignitions

Can cause overvoltages !

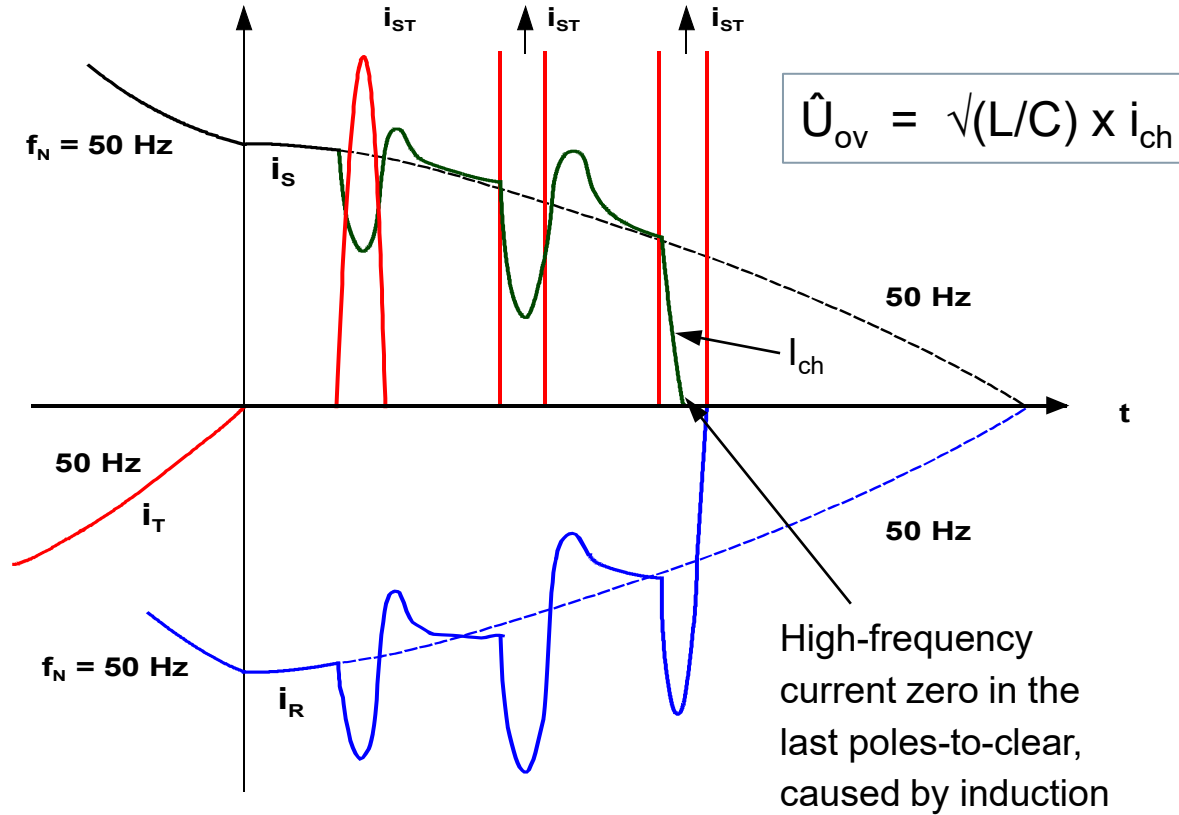

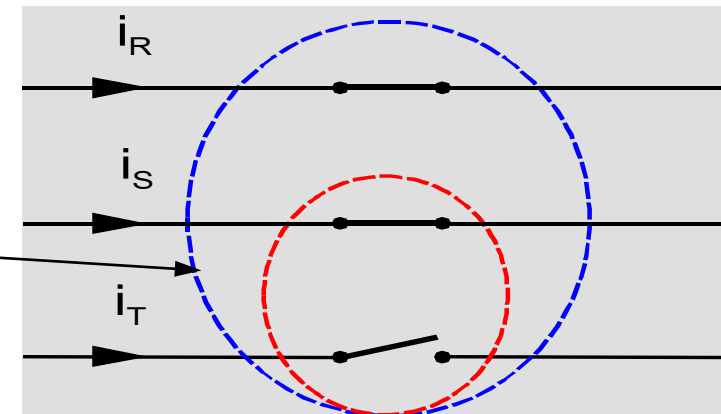- Preconditions to trigger higher surges:
 - contact opening < 0.5 ms prior to current zero
 - inductive current between 20 A to 600 A
- 600 A: limit of virtual current chopping
- >600 A: no virtual current chopping observed
- < 20 A: iron losses damp TRV
- Type and degree of overvoltage depend on network inductances, capacitances



Recommendation for overvoltage protection
→ Refer to application guide HG11.13

Capacitive circuits

- In capacitive circuits the current leads the voltage.
- When interrupting capacitive currents, the capacitance remains charged and keeps the voltage for a certain time.
- A differential voltage between network and capacitor will set up across the switching contacts, which can reach values twice the network voltage.
- When paralleling capacitor banks, very high inrush currents can occur.
- When switching the following transient effects have to be considered:
 - **High recovery voltage,**
 - **Inrush current during switching on**
 - **Voltage increase when switching off filters**



Source: Maschinenfabrik Reinhausen

Capacitive circuits normal operation



For class C2, all circuit breakers comply with the following values acc. to IEC 62271-100.

	Line	Cable	Capacitors	Back-to-back capacitor bank	
Rated voltage U_r kV, r.m.s.	Rated line-charging breaking current I_l A, r.m.s.	Rated cable-charging breaking current I_c A, r.m.s.	Rated single-capacitor- bank breaking current I_{sb} A, r.m.s.	Rated back-to-back-capacitor- bank breaking current I_{bb} A, r.m.s.	Frequency of the inrush making current f_{bi} Hz
7.2	10	10	400	400	4250
12	10	25	400	400	4250
17.5	10	31.5	400	400	4250
24	10	31.5	400	400	4250

Rated back-to-back-capacitor-bank inrush making current – see chapter 3: Technical data



Capacitive current limit for Siemens VCB: 70 % of rated current

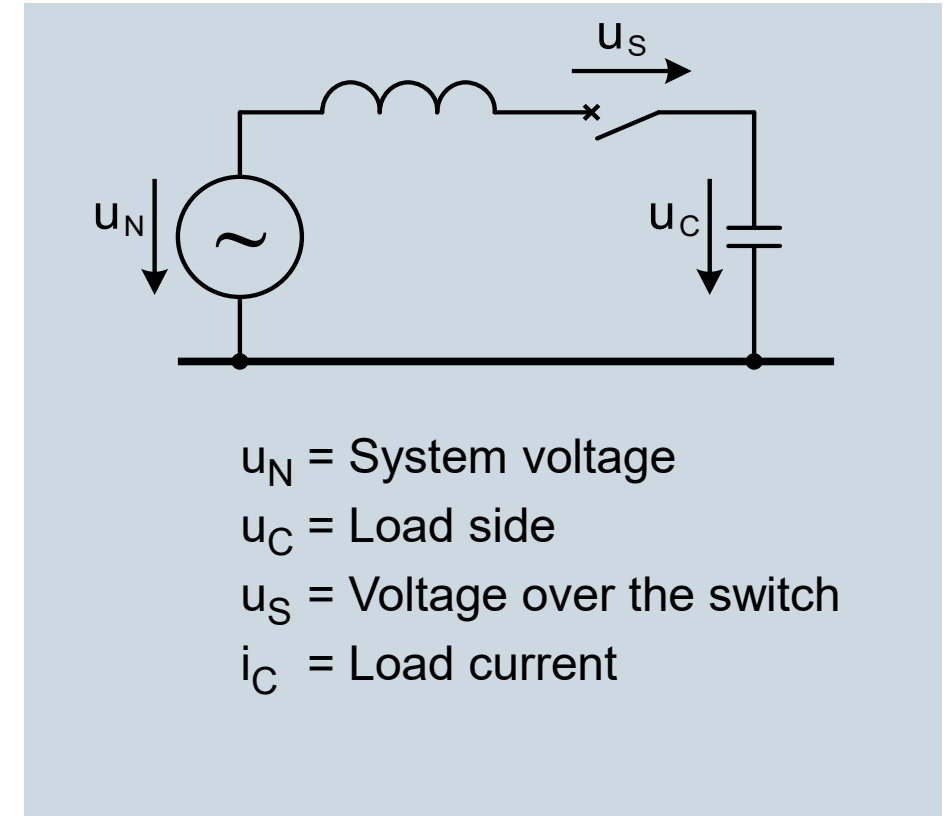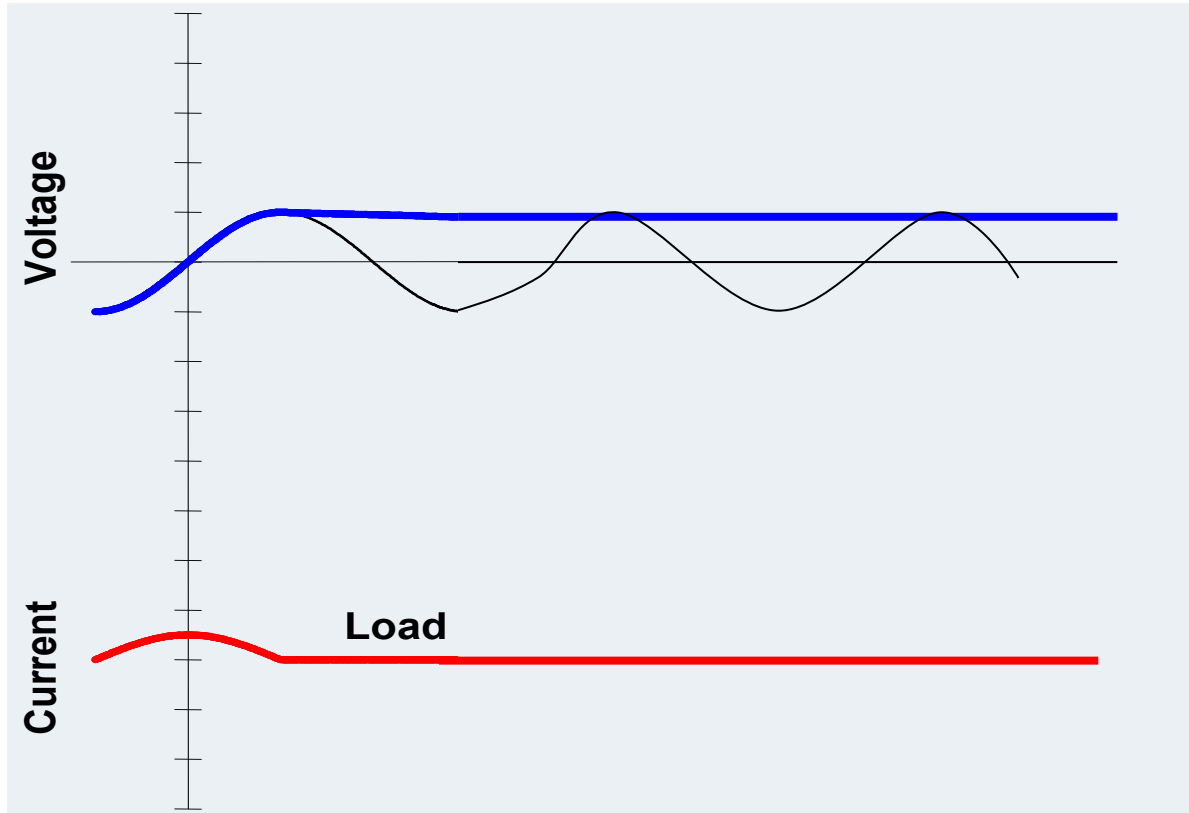C1. Contact system is able to withstand the recovery voltage



The voltage difference across the contacts is twice the peak value of operational voltage.

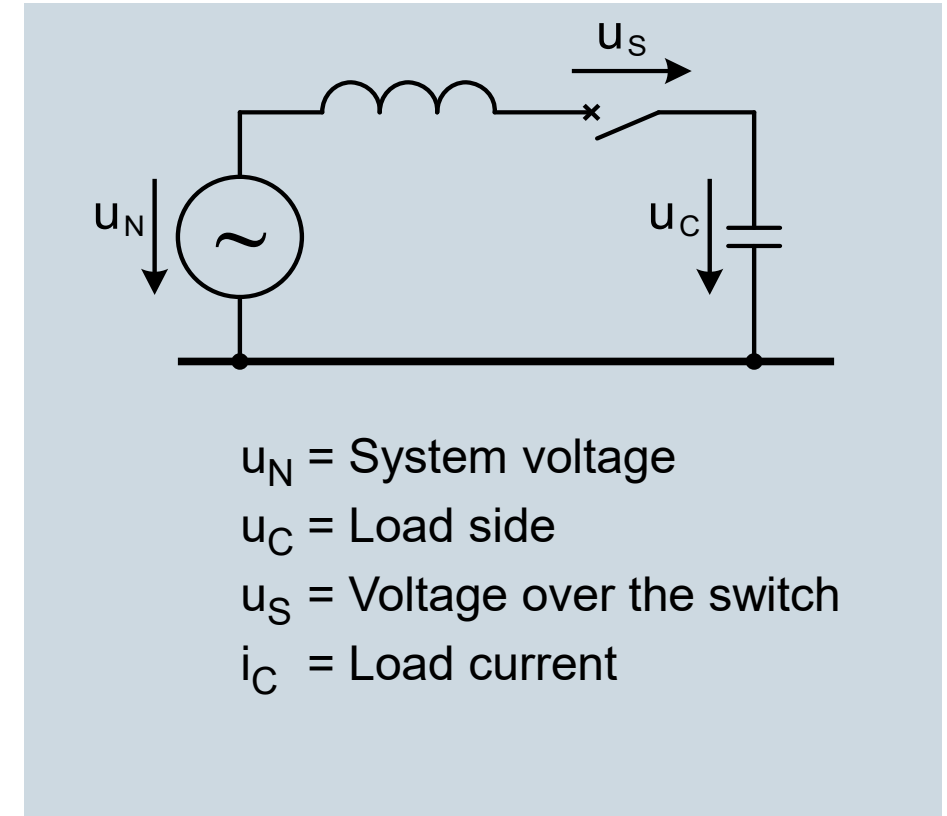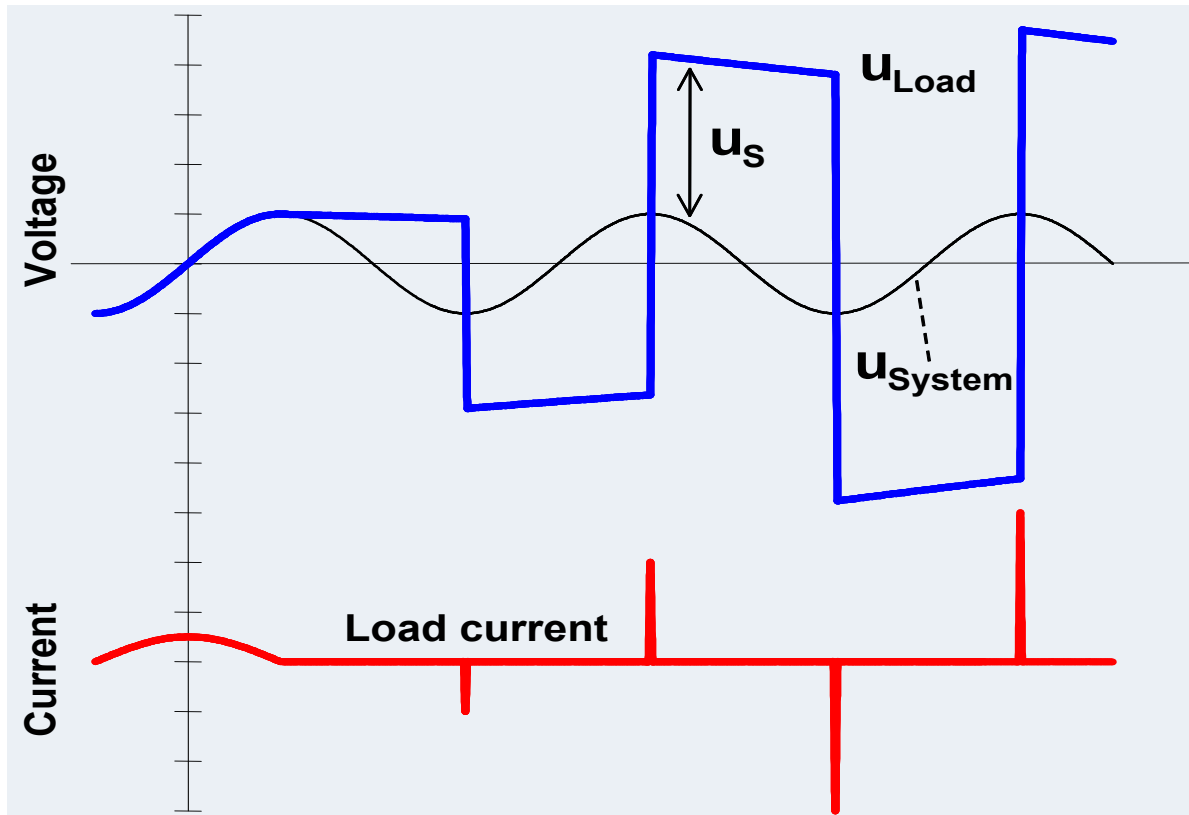
C1. Contact system is not able to withstand the recovery voltage – Re-striking with capacitive current



In case of re-striking the voltage escalates to very high values leading to failing of the breaker.

Breakers for capacitive switching must be re-strike-free. Class C2 required

C2. Paralleling of capacitor banks

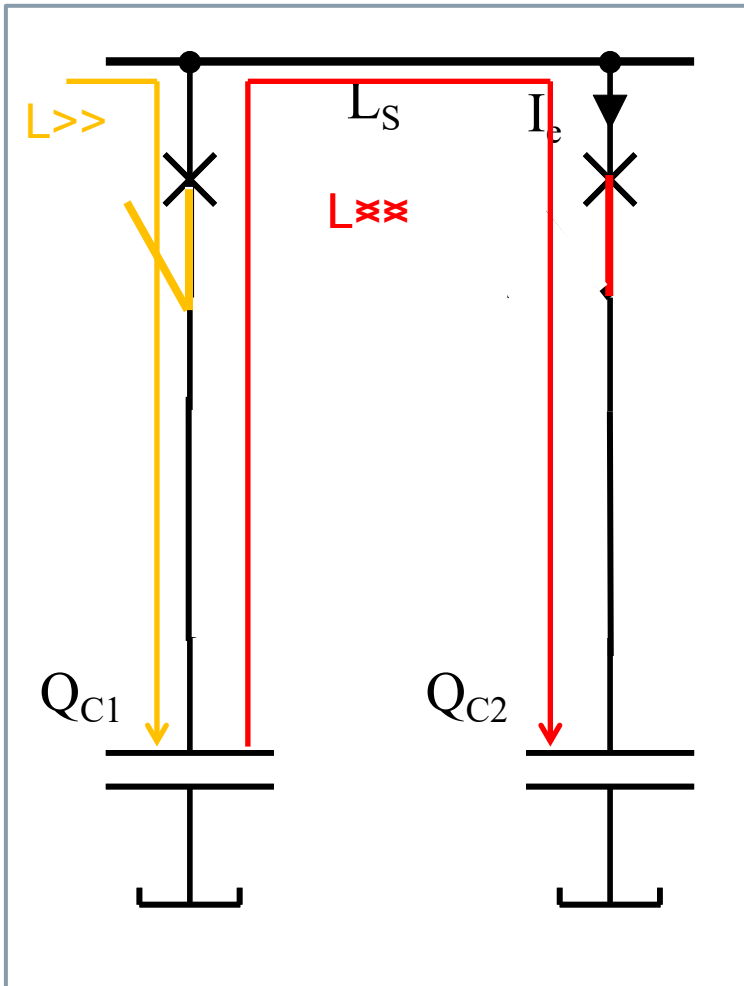

Switching on one capacitor:

- Inrush current will be limited by network inductance ($L \gg$)

Switching on a second capacitor (paralleling):

- Inrush current will be limited by busbar inductance only ($L \ll$)
- Limitation of current by additional coil in series ($L \gg$)

I_e	Inrush current
L_1, L_2	Inductances
L_s	Inductance of bus-bar
Q_{C1}, Q_{C2}	Power of capacitors


Paralleling of capacitor banks

Capacitor banks

- Current: up to $100 \cdot I_{rC}$ (capacitor) permitted
- High amplitude and rate-of-rise of making current
- Very high load on the contact pieces
 - Plate contacts $\hat{I}_e = 10 \text{ kA}$
 - Requirement to IEC $\hat{I}_e = 20 \text{ kA at } 4250 \text{ Hz}$



► **Switching devices must be able to open the partially welded contacts.**

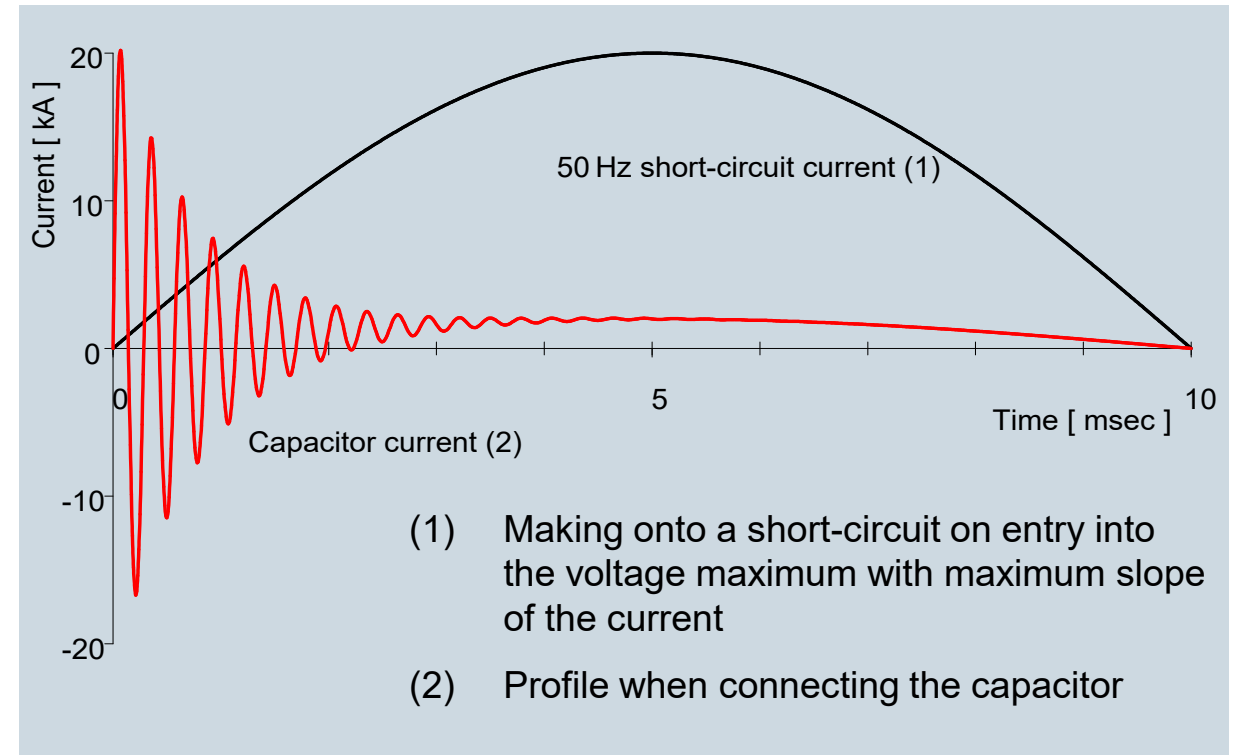- This behaviour is influenced by
 - contact material
 - operating force
 - Quality of VI



→ Back-to-back capability is a rating has to be type tested

C3. Voltages in a filter circuit

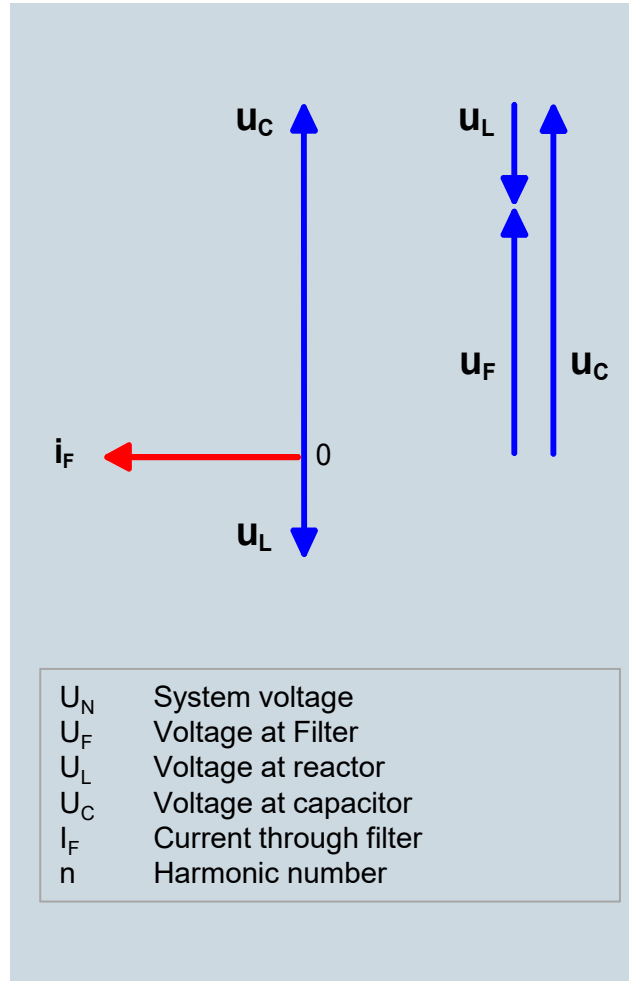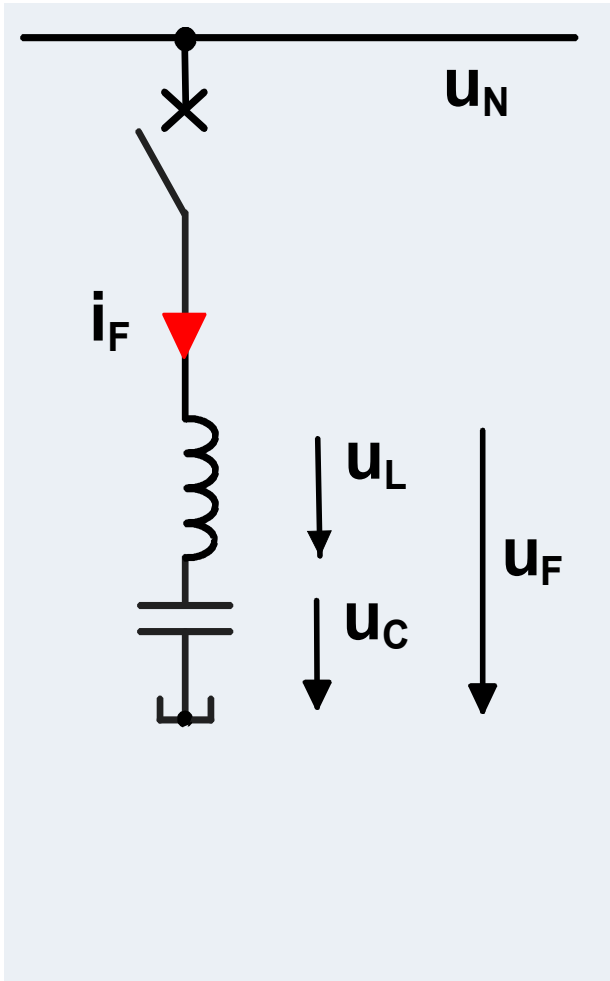

Closed condition:

- Filter and system voltage are identical

Opened condition:

- Filter voltage is equal to capacitor voltage
- Voltage can be calculated by means of harmonic number

$$U_C = U_{N_{\max}} \cdot \frac{n^2}{n^2 - 1}$$

Filter voltage can be higher than system voltage on the bus-bar side

Engineering guide

Application guide for VCB and VC

- Physical / electrical background of applications
- Normal & fault operation
- Limits of application
- Protection measures, e.g. overvoltage protection by surge arresters, RC elements or design



<https://siemens.sharepoint.com/teams/P0000219/SitePages/Projektierungsleitfaden.aspx>

Disclaimer

© Siemens 2022

Subject to changes and errors. The information given in this document only contains general descriptions and/or performance features which may not always specifically reflect those described, or which may undergo modification in the course of further development of the products. The requested performance features are binding only when they are expressly agreed upon in the concluded contract.

All product designations may be trademarks or other rights of Siemens AG, its affiliated companies or other companies whose use by third parties for their own purposes could violate the rights of the respective owner.

| Contact

Christian Heinrich

Product Portfolio Manager

Smart Infrastructure

SI EA PLM MV-AIS C

Nonnendammallee 104

13629 Berlin

Germany

Phone +49 (173) 8527261

Mobile +49 (173) 8527261

E-mail christian.heinrich@siemens.com