

Circuit Colouring with REG

Suitable
for year
6!

To power an electrical component such as REG's speaker or KB2's fan we need the following:

- A power source (like a battery)
- A complete circuit (no gaps)
- Wires connected to the positive and negative ends of the power source

Look at the below circuits and only colour in the electrical components that will have an electrical current running through them.

